



LECTURE ONE

MATHEMATICAL MODELS OF SYSTEMS

1.1 Transfer Function:

The T.F. of a System is the ratio of Laplace Transforms of the output and input quantities, where initial conditions being Zero.

Example 1.1: Derive the T.F. (V_o/V_i) of the below shown circuit.

Solution:

Using voltage divider rule;

$$V_o = V_i \frac{X_C}{X_C + R}$$

Note that $X_C = \frac{1}{j 2 \pi f C} = \frac{1}{s C}$



Therefore; $\frac{V_o}{V_i} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}}$, Simplifying to obtain; $\frac{V_o}{V_i} = \frac{1}{sCR + 1} = \frac{1}{sT + 1}$

Where, $T=RC$.

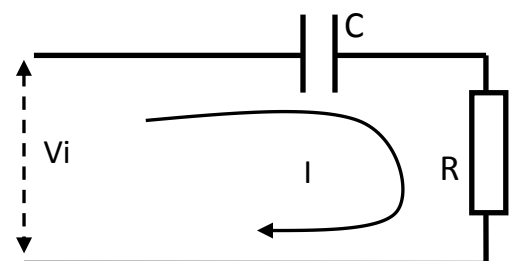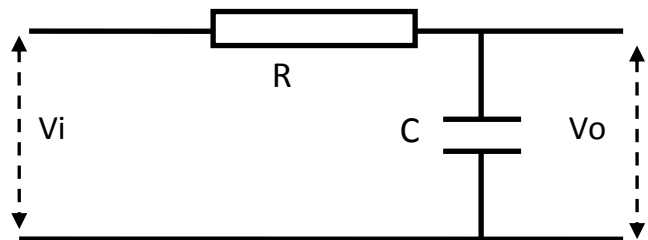Example 1.2: Derive the T.F. (I/V_i) of the below shown circuit.

Solution:

$$V_o = Z_{total} I = I \left(R + \frac{1}{sC} \right)$$






Then;

$$\frac{I}{V_o} = \frac{1}{R + \frac{1}{SC}} = \frac{SC}{SCR + 1}$$

Problem 1.1:

Derive the transfer function (V_o/V_i) for the circuit shown below;

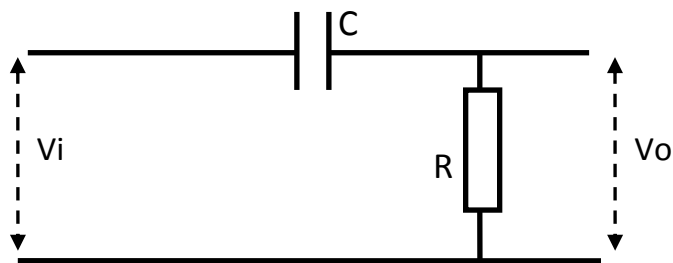

Example 1. 3:

Derive the transfer function (V_o/V_i) for the circuit shown below.


Solution:

$$V_o = V_i \frac{R2}{Z_1 + R2}$$

$$\frac{V_o}{V_i} = \frac{R2}{Z_1 + R2}$$

Where $Z_1 = R1 // X_c$
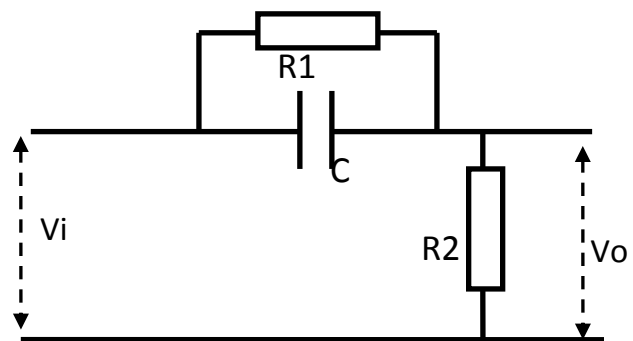
$$Z_1 = \frac{R1 X_c}{R1 + X_c} = \frac{R1 \frac{1}{SC}}{R1 + \frac{1}{SC}} = \frac{R1}{R1CS + 1}$$






Then;

$$\frac{V_o}{V_i} = \frac{R_2}{\frac{R_1}{R_1CS + 1} + R_2} = \frac{R_1 R_2 C S + R_2}{R_1 + R_1 R_2 C S + R_2}$$

Problem 1.2:


Derive the transfer function (V_o/V_i) for the circuit shown below;

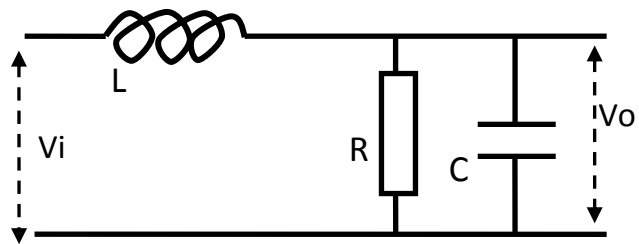

Example 1.4: Derive the transfer function (V_o/V_i) for the circuit shown below;

Solution:

Constructing KVL equations.

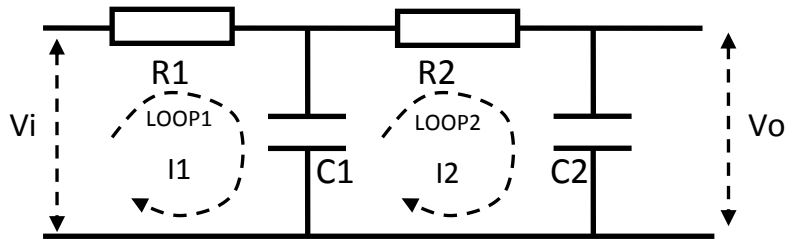

LOOP1:

$$V_i = I_1 R_1 + X_{C1} (I_1 - I_2)$$

$$V_i = (X_{C1} + R_1) I_1 - X_{C1} I_2 \dots\dots\dots (1.1)$$

LOOP2:

$$X_{C1} (I_2 - I_1) + R_2 I_2 + V_o = 0$$

$$(X_{C1} + R_2) I_2 - X_{C1} I_1 + V_o = 0 \dots\dots\dots (1.2)$$



Now since $V_0 = I_2 X_{C2}$ then substituting in equation (1) will result in:

$$V_i = (X_{C1} + R_1) I_1 - X_{C1} (V_0 / X_{C2})$$

$$I_1 = \frac{V_i + \frac{X_{C1}}{X_{C2}} V_0}{X_{C1} + R_1} \dots\dots\dots (1.3)$$

then substituting equation (3) together with $V_0 = I_2 X_{C2}$ in equation (2), get;

$$(X_{C1} + R_2) \frac{V_0}{X_{C2}} - X_{C1} \frac{V_i + \frac{X_{C1}}{X_{C2}} V_0}{X_{C1} + R_1} + V_0 = 0$$

$$\frac{(X_{C1} + R_2)}{X_{C2}} V_0 - \frac{X_{C1}^2}{X_{C2} X_{C1} + R_1 X_{C2}} V_0 + V_0 - \frac{X_{C1}}{X_{C1} + R_1} V_i = 0$$

$$\frac{V_0}{V_i} = \frac{\frac{X_{C1}}{X_{C1} + R_1}}{\frac{(X_{C1} + R_2)}{X_{C2}} - \frac{X_{C1}^2}{X_{C2} X_{C1} + R_1 X_{C2}} + 1}$$

$$\frac{V_0}{V_i} = \frac{X_{C1}}{\frac{(X_{C1} + R_1)(X_{C1} + R_2)}{X_{C2}} - \frac{X_{C1}^2}{X_{C2}} + (X_{C1} + R_1)}$$

$$\frac{V_0}{V_i} = \frac{X_{C1} X_{C2}}{(X_{C1} + R_1)(X_{C1} + R_2) - X_{C1}^2 + X_{C2} R_1 + X_{C2} X_{C1}}$$

$$\frac{V_0}{V_i} = \frac{X_{C1} X_{C2}}{X_{C1}^2 + R_1 R_2 + R_1 X_{C1} + R_2 X_{C1} - X_{C1}^2 + X_{C2} R_1 + X_{C2} X_{C1}}$$

$$\frac{V_0}{V_i} = \frac{X_{C1} X_{C2}}{R_1 R_2 + R_2 X_{C1} + R_1 X_{C1} + X_{C2} R_1 + X_{C2} X_{C1}}$$




Therefore;

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC_1} \frac{1}{sC_2}}{R_1 R_2 + R_2 \frac{1}{sC_1} + R_1 \frac{1}{sC_1} + \frac{1}{sC_2} R_1 + \frac{1}{sC_1} \frac{1}{sC_2}}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{C_1 C_2 R_1 R_2 s^2 + R_2 C_2 s + R_1 C_2 s + R_1 C_1 s + 1}$$


Problem 1.3:

Derive the transfer function (V_o/V_i) for the circuit shown below;

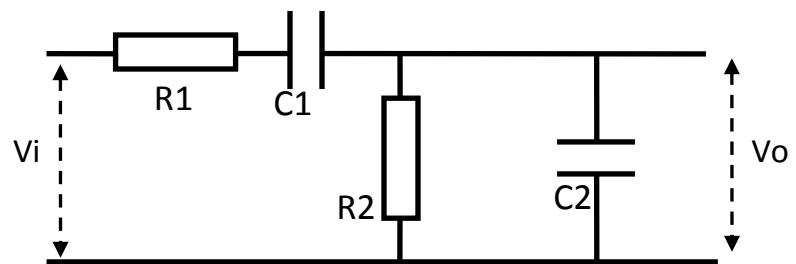

Problem 1.4:

Derive the transfer function (V_o/V_i) for the circuit shown below;

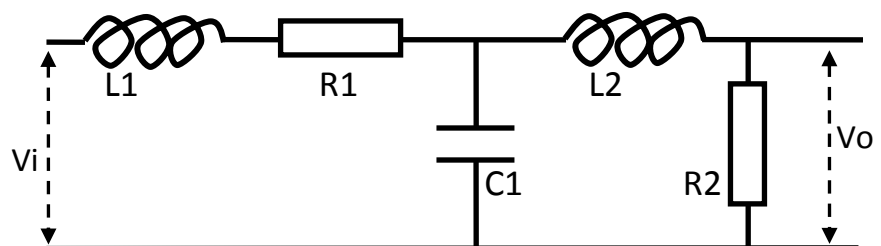

**Problem 1.5:**

Find the transfer function (V_o/V_i) for the circuit shown below;

